

# How to Use Dubbing Cables and Remove Disk Protection

In volume 2 of this text, dubbing cable creation was introduced and was largely popular, but we believe many readers found it fairly challenging.

However, in the above circumstances, the diagrams, pictures, documents, and the like contained insufficient sections and it was indicated to us that the beginners out there understood very little.

Accordingly, this how-to guide\* will explain the construction and usage of the dubbing cable if followed exactly.

Furthermore, the previous issue's circuit proved unstable in some cases and this has been improved.

Also, we'll look at the method for removing the protection introduced on newer models produced after last autumn.

#### **Dubbing Cable Creation How-To Guide**

First of all, to use the dubbing cable, here's what is necessary.




Famicom Disk System
 (RAM adapter not used with the cable)

• • • • • • • 2 sets

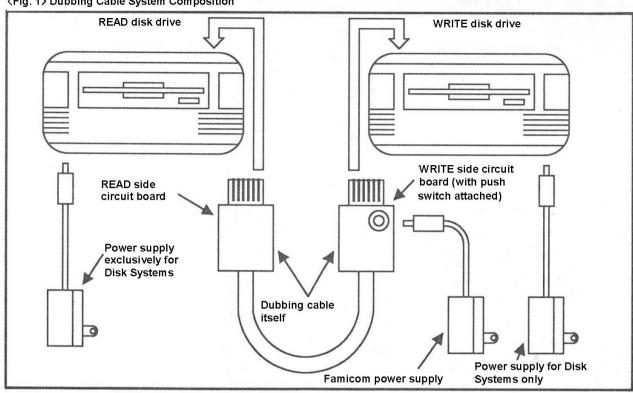2) Famicom Disk System AC adapter. Or, size C batteries - - 2 sets

⟨Fig. 1⟩ Dubbing Cable System Composition



- Assembled "dubbing cable" . . . . . . . . . . 1 set
- Famicom AC power adapter (for use with dubbing cable) . . . . . . . . . . . 1 set

The equipment above is required for the dubbing of a disk card.

Prepare to insert an original game disk card and a blank disk card. (Fig. 1)

#### **▶** Dubbing Cable Production

Please look at Vol. 2 in detail.

Here, figures (Fig. 2~4) are added to that which was omitted from Vol. 2. Please see figure 5 for each of the parts used.

When doing the wiring work, pay close attention to the detailed wiring diagram.

Avoid sweet potato soldering\*. solder attached to the soldering iron will oxidize immediately and change color.

After wiping the old solder from the iron with some wet tissue paper and then using fresh new solder, you should be able to conserve solder and use a minimum amount\*\*.

With plenty of soldering practice you will polish your soldering skills.

Please be careful and certain when wiring the connectors that insert into the disk drives in accordance with the above diagram. This requires special attention since there are many signals that may not operate properly due to mistakes here.

for the method to make connectors themselves introduced in Vol. 2, it may be too difficult and frustrating for many people to do, but you can mail order for completed connectors, introduced later.

#### Dubbing Cable Usage


When the wiring and assembling of the dubbing cables are done, verify there are no wiring errors, then connect the power sources as shown in Fig. 1.

Then, prepare a blank disk card and an original disk card.


\*It appears "imo handa," or, "sweet potato soldering" (I guess. I don't think "imo" has any other definitions) is a term that is generally used to mean bad soldering, or faulty soldering technique. I would welcome any correction on this, but I believe it might not just refer to overheating the solder with the iron, causing the solder to change color but possibly also just generally bad connections in the soldering. Over-oxidizing the solder (generally done via excessive over-heating) causes weak solder joints, which is why it is recommended to avoid this.




<Fig. 2> Dubbing Cable Wiring Diagram

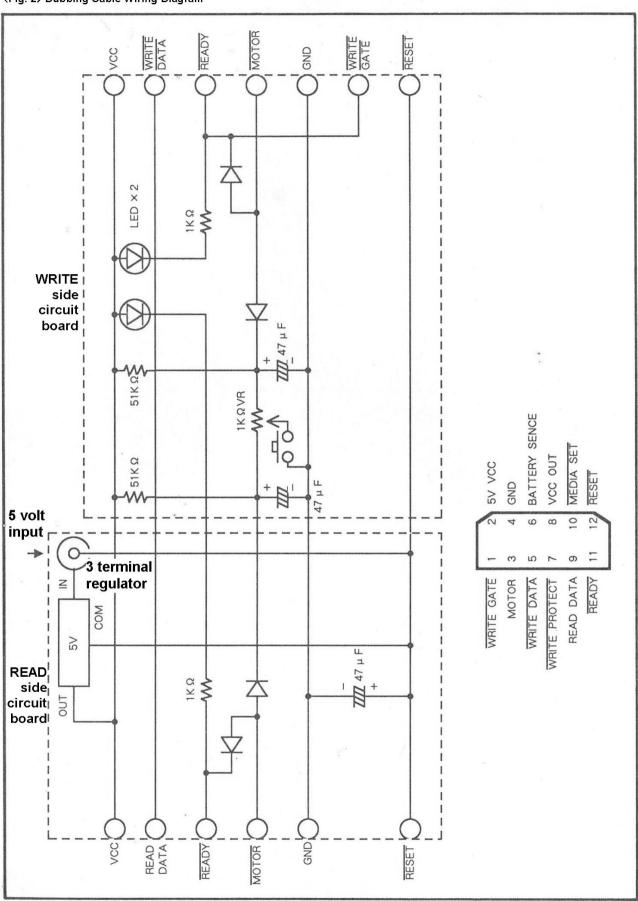

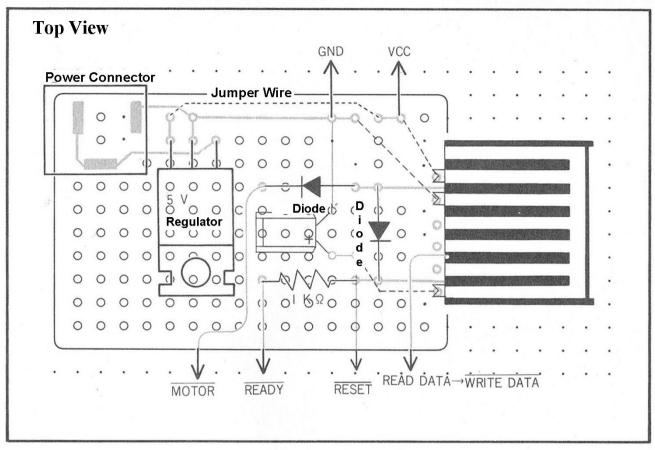⟨Fig. 3⟩ Connector Wiring Diagram (READ Side)




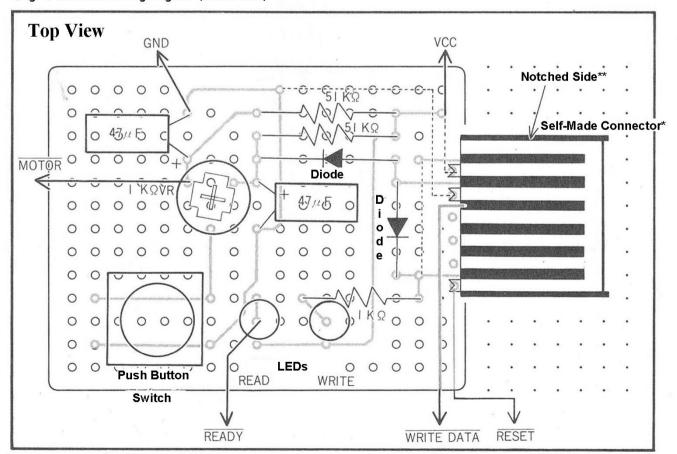⟨Fig. 4⟩ Connector Wiring Diagram (WRITE Side)



<sup>\*</sup>Instructions to make these are in Volume 2, the previous issue.



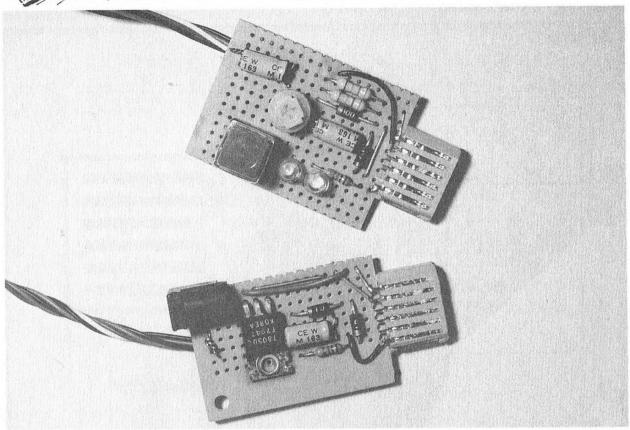

(Photo 1) WRITE Side and READ Side

Follow these steps to perform the dubbing.

#### <<Step 1>>

Set the READ side disk drive with the original (game) disk that you want to back up, and set the WRITE side disk drive with the disk (a blank disk is OK) you want to write to.

#### <<Step 2>>

Depress the push switch on the WRITE side for about 3 seconds.

#### <<Step 3>>

Adjust the variable resistor on the WRITE side board so that the two LEDs on the board shine simultaneously.

If they shine simultaneously, backup will happen automatically.

#### <<Step 4>>


Flip the disk cards of READ and WRITE sides over after this and repeat steps 2 and 3 to copy the other side of the disk cards.

By following the above steps, the dubbing of the game disk is done.

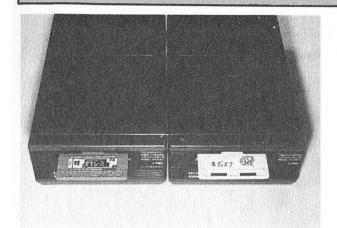
### Dubbing Cable Strengths and Weaknesses

The principle of this system is the same as the dubbing of a cassette tape. Therefore, if dubbing is repeated by this method through successive generations of disk cards, data degradation occurs and eventually, further copying becomes impossible. In fact, a "great-grandchild" copy is the absolute limit, but try to copy directly from a parent disk when at all possible.


Although this is a weakness of the dubbing cable, as a strength, backup tools like "Disk Hacker," and so on, can copy with just one disk drive, and since the data of an original disk is not separately read by the CPU itself of the Family Computer, it will



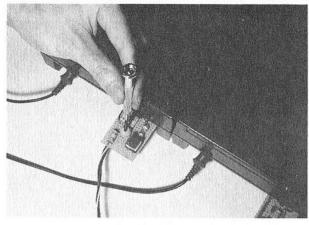
<Photo 2> The disks are set to the READ and WRITE sides. respectively.



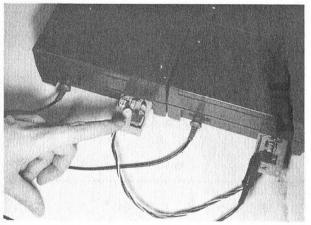
<Photo 4> The variable resistor is adjusted so the WRITE side board's LEDs shine simultaneously


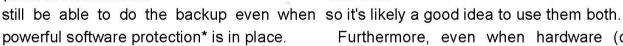
<Photo 3> The push switch on the WRITE side board is pushed for about 3 seconds.



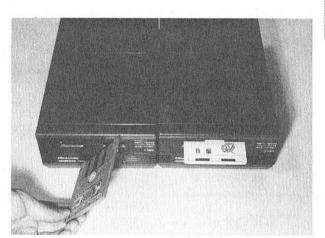"Disk Hacker," the copy becomes the same to remove it, which we'll now discuss. as its parent, combining the tools' strengths,



<Photo 5> If the outcome is OK, flip the disks to copy the

Furthermore, even when hardware (cir-Also, even when a disk card backed up by cuited) protection is integrated into the drive, the cable has degraded, if re-backed up with all that's needed is some simple modification

#### Use of the Newer Protected Models is Also OK Now!! How to Make the Disk Protection Takeover Board for the Newer Model

When the dubbing cable above is used, it's assumed the disk drive isn't protected, so we'll now examine how to address this.

#### **♠** A Look at How to Remove the Protection

This is carried out as follows.


Open the disk system's case, and remove the circuit board below the battery box to examine the number on it. (Fig. 6)

If this number is "01"~"03" then there is no protection. Reassemble the case and use it as before.

If it is "04" or "05," perform the wiring




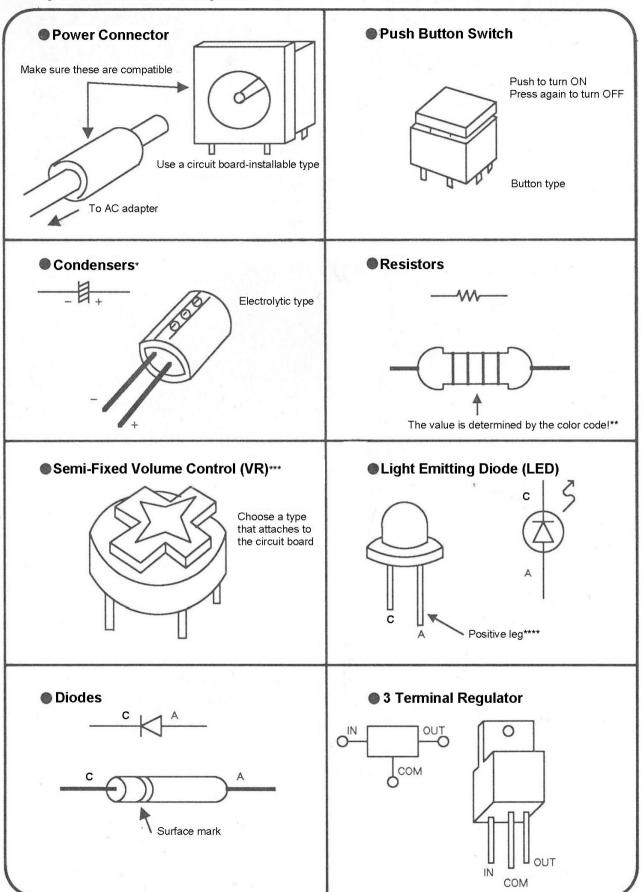(Fig. 5) Parts Used For the Dubbing Cable




<sup>&</sup>quot;Also known as capacitors.
"It is, highly unlikely a store will need the color code on a resistor to find it, but it sometimes helps to know what they are and what they mean. Just give them the values denoted in the diagrams.
"It he anode, or positive leg is longer than the cathode, or negative leg.
"It he anode, or positive leg is longer than the cathode, or negative leg.
"It have been and the service of the temporary of the time of the temporary of the tempor

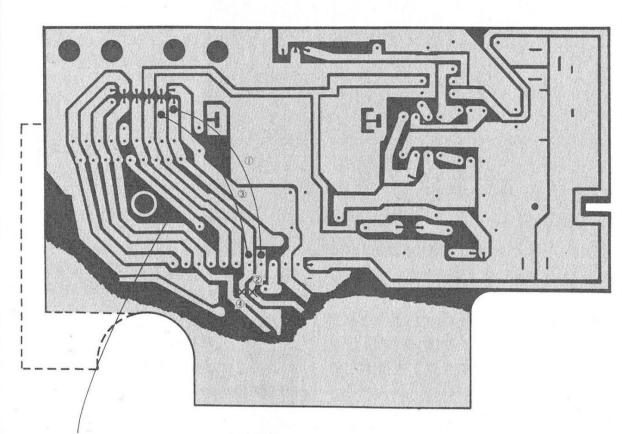⟨Fig. 6⟩ Section on Cutting Off the Protection




If the number written here is 04, connect 1 and cut 2.

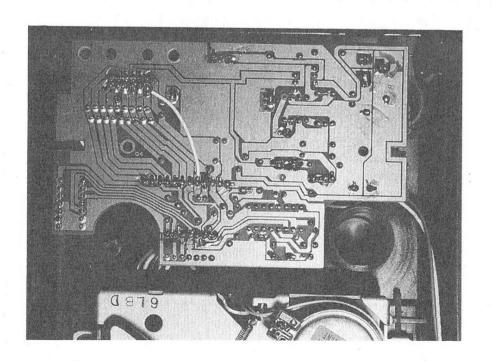If it is 05, connect 1 and 3 and cut 2 and 4



## TO COLORA

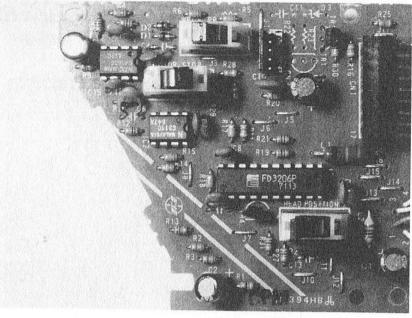

<Photo 6> Look into the disk system from the top and if the IC number is FD3206 it is a newer protected model!!

and cut the pattern shown in Fig. 6, which will remove the protection.

In addition, if the READ side is also protected, it is not necessary to remove that protection when the dubbing cable is used with it.

Remove the protection only from the WRITE side.

## How to Remove the Protection on the Newer Models

Although the above is the same as what


was introduced in Vol. 2, the newer protected model came out around fall of last year.

Look into the disk unit from the top (Photo 6).

The IC is visible from here, and if the IC number is FD3206, it is the newer protected model (if it's FD7201 then it's OK).


Since demand was good with retailers, the older models have been selling out, and it's thought that the newer protected models are common now. However cheap they may be, it's safest to pass them by (if you intend to use them for the READ sides only without modification, then that's OK).

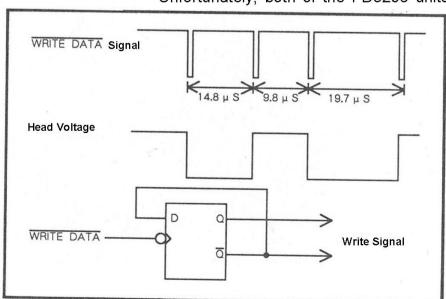Unfortunately, both of the FD3206 units I




<Fig. 7> Structure of the Takeover Board
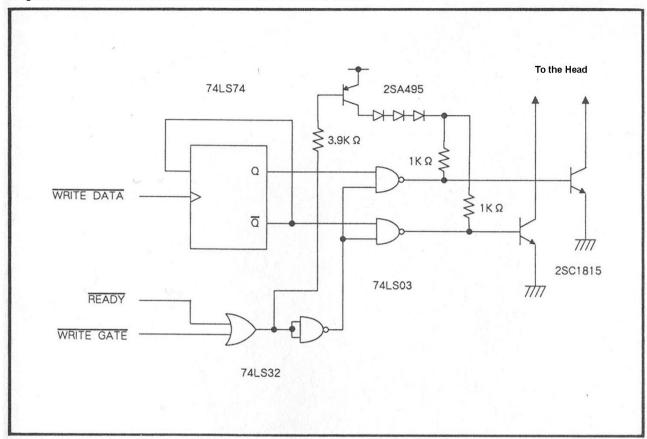
<Fig. 8> The Takeover Board Circuit Attached to the Protection Circuit




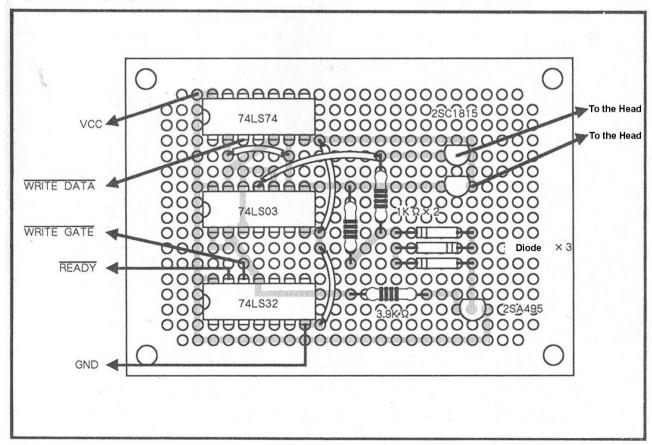
<Fig. 9> The Wiring Diagram of the Takeover Board Itself





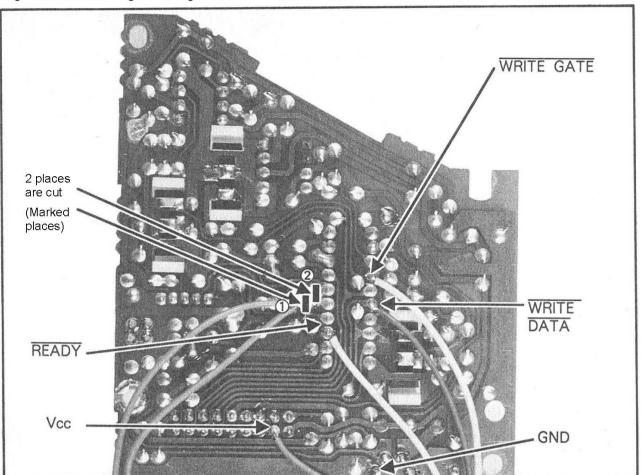
<Fig. 10> Section Showing the Cutting Pattern for the FD3206 Drive Board



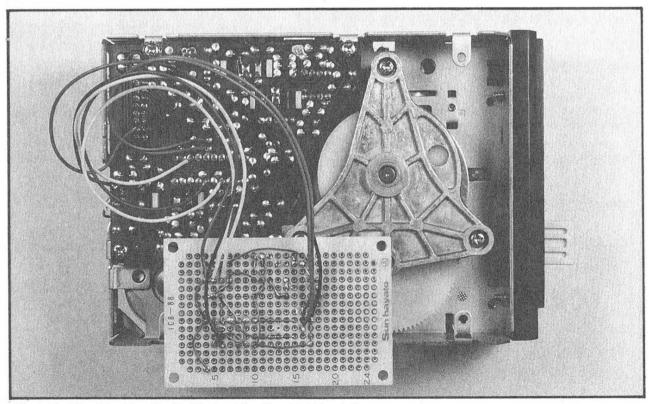
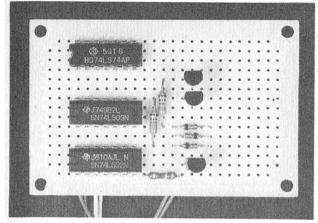
<Photo 7> The Drive Board is Modified and the Signal is Extracted.



<Photo 8> The Completed Takeover Board.

obtained had to be converted for WRITE side use.



#### **♠** About the Takeover Board

contents of the IC the inconvertible, what the IC does is reconstructed by a logic circuit, as the IC can only be taken over externally.

The voltage of the head of the disk drive divides the WRITE DATA signal (Figure 7).\*

In other words, it is necessary to let WRITE DATA input to the D flip-flop, and output right to the drive head.\* Simple, isn't it? A hacker doesn't have to be a megagenius!\*\*

Fig. 8 adds a protection circuit so if there is a shock at WRITE GATE, READY, or if the power supply is turned on or off, it will not corrupt the disk card data. (Photo 7)




#### Takeover Board Installation

Remove the disk unit and open the metal cover on the reverse. At this time, please don't loosen the screw visible from the circular hole by any means.

Cut the pattern near pin no. 14 and pin no.15 of the FD3206 (the signals that go to the head).

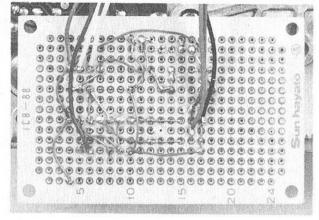Do the wiring as shown in Fig. 10. Also, with the modification, rest assured you can



<Photo 9> Takeover Board (Reverse Side)

enjoy your games as before.


Moreover, this modification is effective with Disk Hacker. Kosodate Gokko. Tonkachi Editor, Quick Hunter, etc.

Those who want pre-made connectors (photo 9)\*\*\* shown in the article or blank disks need to write the following by registered mail. The price is 900 yen (postage included) for 1 two-piece set of pre-made connectors.

©10 blank disks (ZAP brand) are 4800 yen (for up to 40 include 900 yen postage, for 50 and up postage is included, and for 100 and up @ 450 yen each, postage is included).
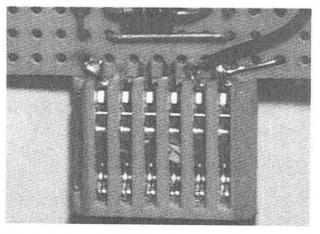
#### @Address

〒165 Nogata, Nakano-ku, Tokyo, 6-17-5 Iwade Kouporasu 202 "Angel Software" 03-223-1757



⟨Photo 10⟩ Finished Self-Made Connector

don't assume to completely know how these circuits work, but I believe this is the correct translation for these sections, however ambiguous it may be to a beginner. Also, a D-type (or data type) flip-flop circuit is a standard form of logic circuit (flip-flops are meant to alternate the state of a signal between two states). The D also refers to one of the two inputs to a D-type flip-flop circuit.

<sup>\*\*\*</sup> I think they meant Fig. 10, But maybe they sent you the whole board. Who knows?